

1/7

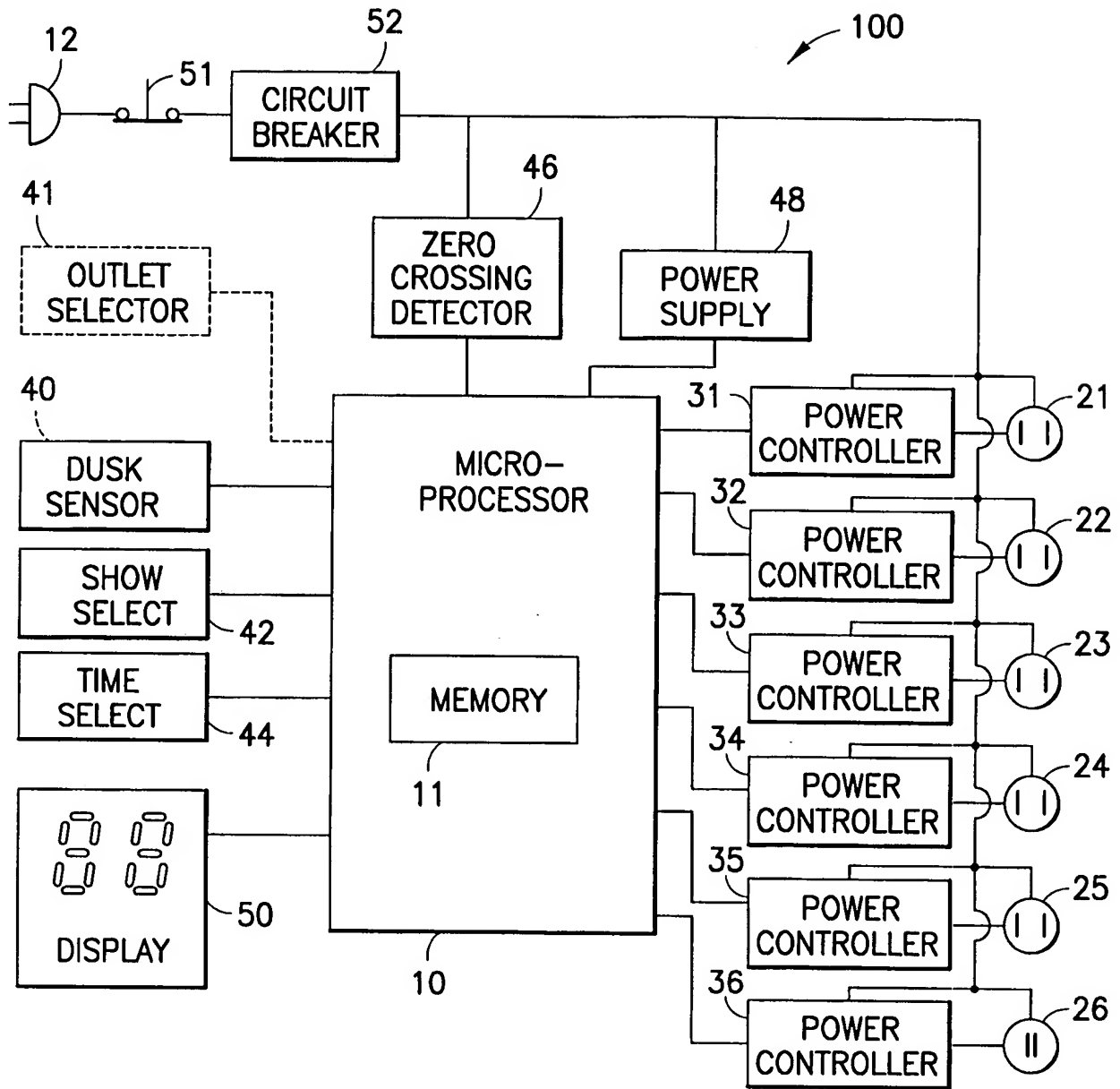


FIG.1


TIMER SETTING:

ALWAYS ON—STEADY ILLUMINATION  
 OFF  
 DUSK—ON FOR 2 HOURS  
 DUSK—ON FOR 4 HOURS  
 DUSK—ON FOR 6 HOURS  
 DUSK—ON FOR 8 HOURS  
 DUSK TO DAWN  
 OUTLET OVERLOAD

DISPLAY WILL READ:

AO  
 OF  
 2H  
 4H  
 6H  
 8H  
 dd  
 ER

FIG.3

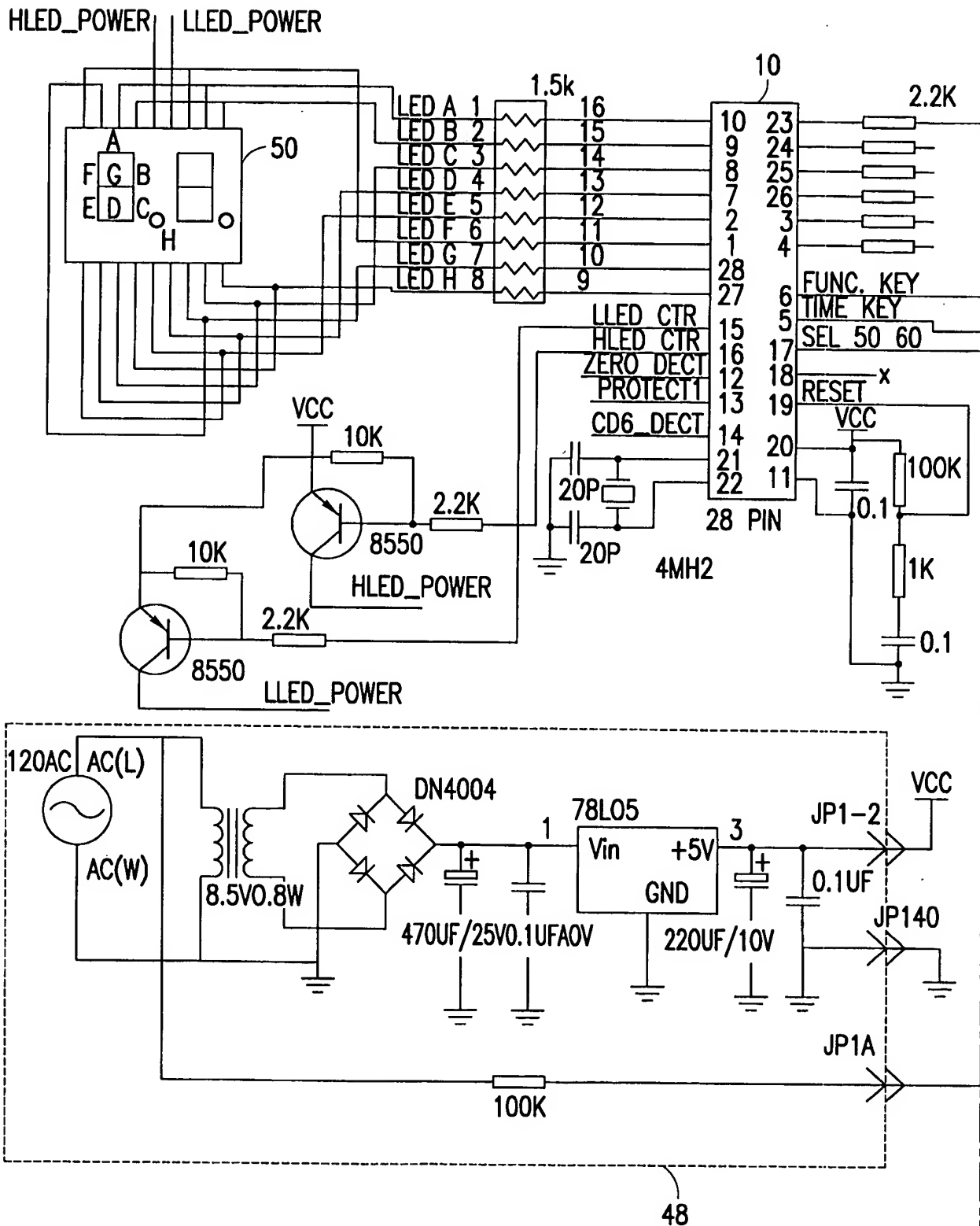

**FIG. 2A**

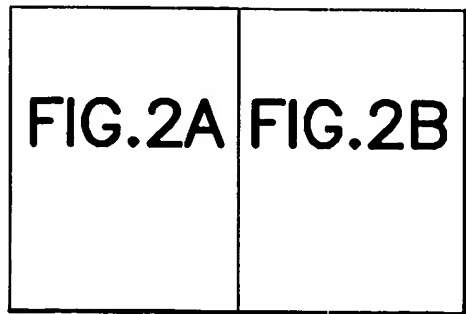


FIG.2

| <u>SHOW<br/>NUMBER</u> | <u>SHOW<br/>DESCRIPTION</u>   |
|------------------------|---|
| 01                     | STEADY ON   |
| 02                     | Steady On (no effects)<br>CASCADING FLASH/FADE ON   |
| 03                     | Progressive/3 Flashes and Fade On/Chase Up<br>FLASH/FADE ON   |
| 04                     | Progressive 8 Flashes/Progressive Fade On/Flash Twice/Down to Steady On<br>FADE UP AND DOWN   |
| 05                     | Progressive Fades On/Steady On/Regressive Fades Off to Total Off<br>MEDIUM SPEED FADE ON  |
| 06                     | Progressive Med. Speed Fade On/Cycles Twice/Steady On<br>SLOW FADE ON   |
| 07                     | Progressive Slow Fade On/Off/Steady On<br>RANDOM FLASHING AND FADING  |
| 08                     | Random Flash/Random Fade On in Random Sequence (ideal for Halloween Decorating)<br>VARIABLE CHASING   |
| 09                     | Progressive Slow Chase/Speeds Into Fast Chase Up/Regressive Chase/Sequence Chase Up/<br>Sequence Chase Down/Progressive Chase/Regressive Chase<br>CASCADE CHASING |
| 10                     | Progressive Medium Speed Chase Up -9 cycles<br>CASCADE CHASING UP AND DOWN  |
| 11                     | Progressive Medium Speed Chase Up/Progressive Medium Speed Chase Down<br>FAST CHASING   |
| 2                      | Progressive Fast Chase<br>CASCADING FADE ON/FADE OFF  |
| 3                      | Progressive Fade On To Steady On/Progressive Fade On to Off<br>3 X 2 CASCADING FADE ON/FADE OFF   |
|                        | Outlets 1&2, 3&4, and 5&6 in tandem - Fade On To Steady On/Progressive Fade Off to Off/Cycles   |

**FIG.4A**

14 CASCADE ON/STEADY ON/CASCADE FADE OFF  
 Progressive Slow Chase to Steady On/Regressive Slow Chase to Off/2 Cycles  
 15 CASCADING FADE ON/STEADY ON/CASCADE FADE OFF  
 Progressive Fade to Steady On/Regressive Fade to Off/1 Cycle  
 16 RANDOM FLASH  
 Random Sequence of Slow Flash to Fast Flash  
 17 3 X 2 CHASING  
 Outlets 1&2, 3&4, and 5&6 Progressive Chase in Tandem  
 18 4 OUTLETS FADE UP & DOWN (OUTLETS 5 AND 6 STEADY ON)  
 Outlet 1 thru 4 Progressive Fade On to Steady On in Tandem/Progressive Fade to Off  
 Outlets 5&6 are Steady On Function (ideal for using animated lighting or chasing lights – these  
 outlets will not interfere with the functions of lights using their own control boxes or motors)  
 9 ALL PROGRAMS 01–18 IN SEQUENCE  
 All SHOWs play in Sequence – Starting 02 Up to 18 for maximum presentation of effects

FIG.4B

|        |
|--------|
| FIG.4A |
| FIG.4B |

FIG.4

6/7

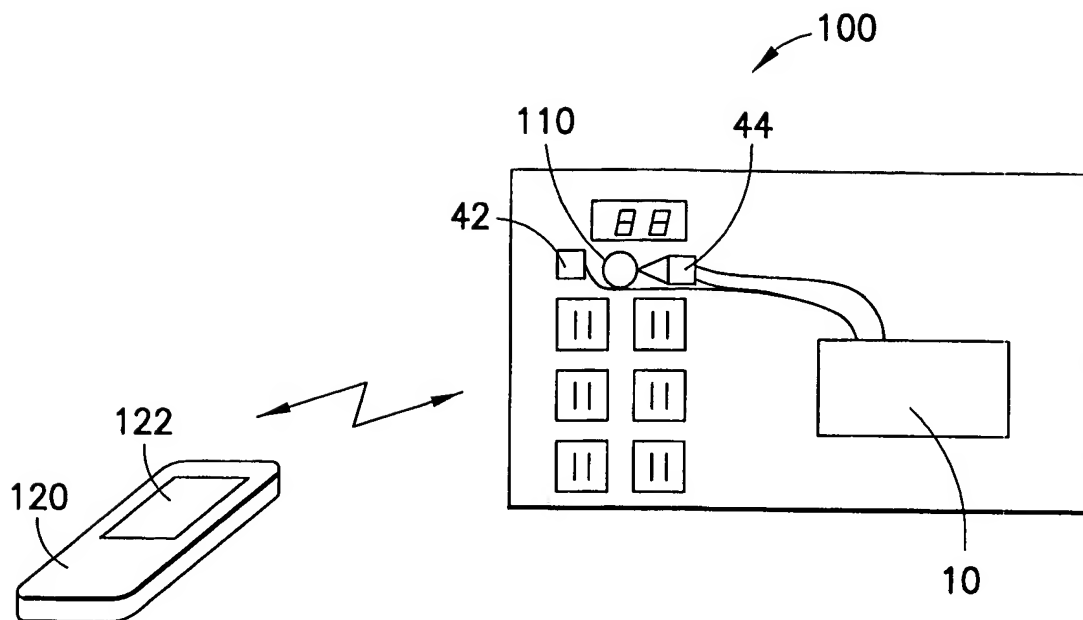


FIG. 5

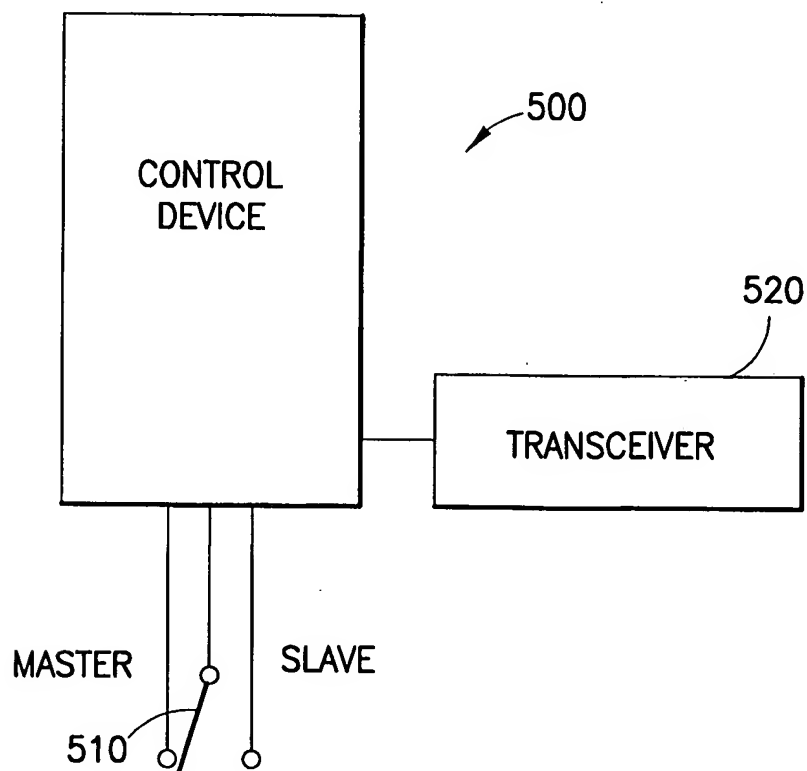


FIG. 7

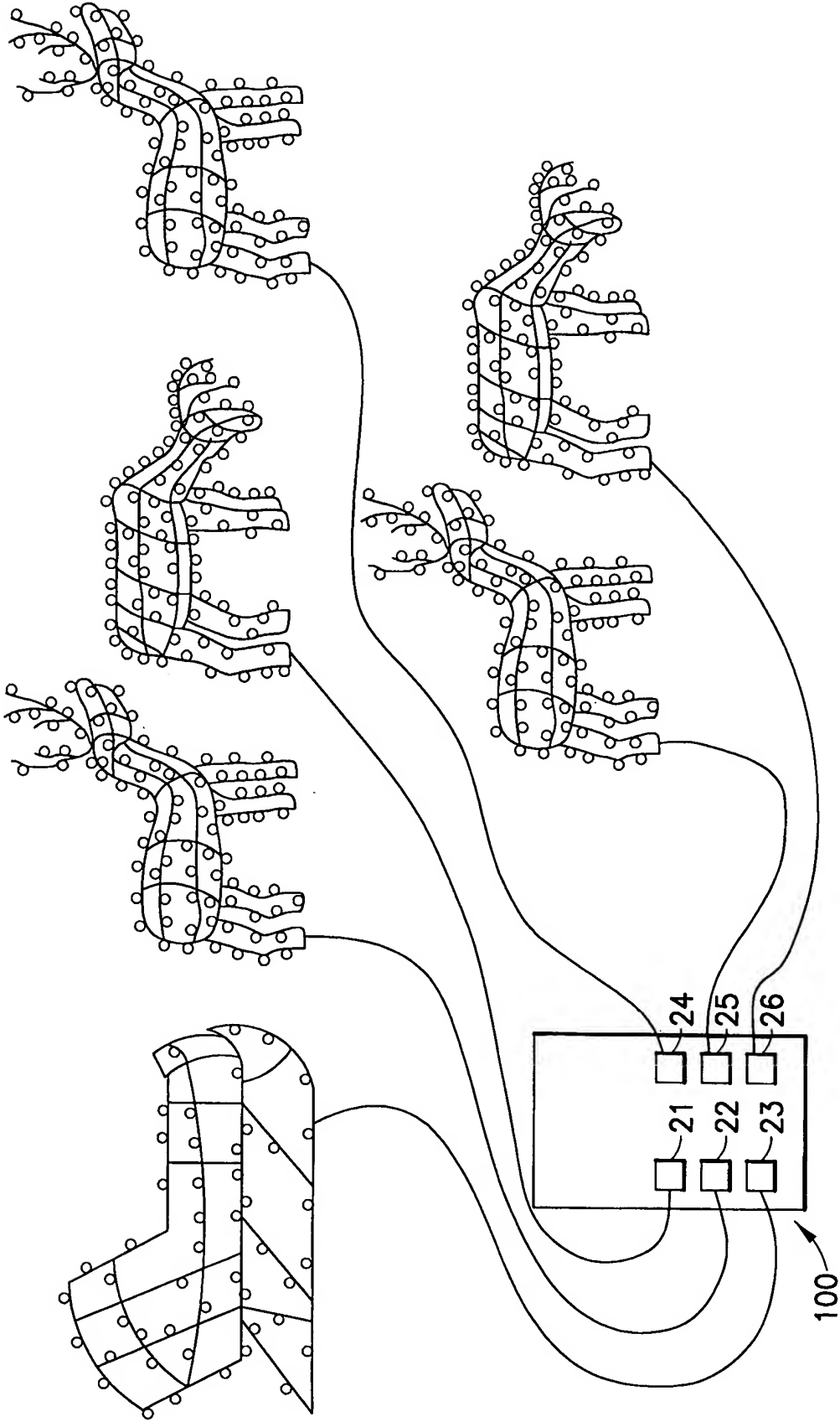


FIG.6